

Date: _____

P. No: _____

Oriental Institute of Science

Technology, Bhopal

Department
OF

Computer science AND Engineering

LAB MANUAL (CS404)

Name - Antaryami Singh

Enroll no. → 0105CS203D03

course code → CS404

Course → Computer org. & Architecture.

Session → JAN-JUN 2021

Section → 'B'

Experiment - 1

Date _____
P. No. _____Objective :- Study of multiplexer and demultiplexer

Theory :-

1) multiplexers :-

A multiplexer is a network that has many inputs and one output, and the value of the o/p will be the value of one of inputs which will be decided by some select lines. The simplest Type of multiplexer is two to one line data multiplexer.

Let A be one of the inputs and B is the other input and Y is the output as in Fig. (1) and S is the select line then

 


Fig. (1)

Two to one line multiplexer.

$Y = A$ if select = 0.

$Y = B$ if select = 1.

The logic circuit diagram of the two to one line multiplexer is shown in Fig. (2)

 


Fig (2)

logic circuit of two to one line mux.

⇒ Example: Design the following expressions using multiplexers.

No. of variables = 3

$$F(A, B, C) = \bar{A}C + \bar{B}C + ABC$$

⇒ solution: - no. of variables = 3, it is better to use 4-to-1

Line multiplex, i.e.

No of selection lines = no of variables - 1.

Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

2.7) Demultiplexers—

A demultiplexer basically reverse of the multiplexer function. It is take data from one line and distribute them to given no. of output lines. fig 13) shown a one to four line demultiplexer circuit.

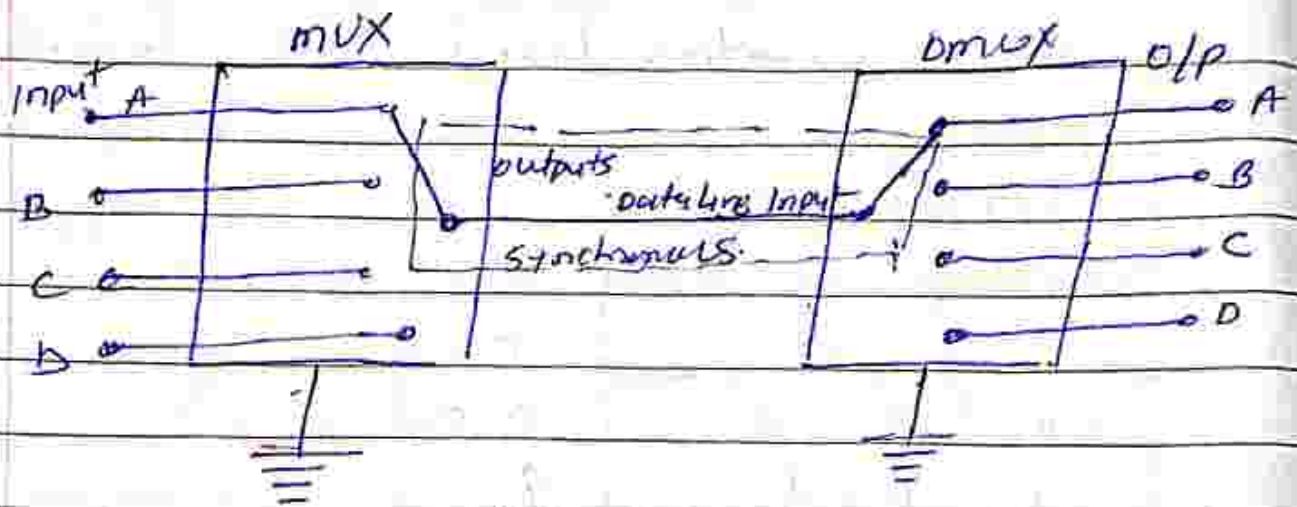


fig (3)

Experiment-2

⇒ study of Half Adders and full adders


Theory:-

Half adder:-

A Half adder has two inputs for the two bits to be added and two outputs one from the sum 's' and other from the carry 'c' into the higher adder.

position. above circuit is called as a carry signal from the addition of the less significant bits sum from the X-OR Gate to the carry out from the AND Gate.

⇒ Logic Diagram :-

 

Truth Table:


A	B	CARRY	SUM
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

2) Full adder :-

A full adder is a combinational circuit that forms the arithmetic sum of input; it consists of three inputs and two outputs. In full adder sum o/p will be taken from X-OR gate, carry output will be taken from OR gate.

Logic Diagram :-

Full adder using Two Half adder :-

 

Tenth Table 3 -

A	B	C	CARRY	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Experiment \Rightarrow 3Objective 3 -

① study of Half subtractor
and full subtractor.


Theory :-Half subtractor 3 -

The half subtractor is constructed using XOR and AND gates. The half subtractor.

Has two input and two outputs.
The outputs are difference and borrow. The difference can be applied using X-OR gate, borrow output can be implemented using an AND gate and an inverter.

→ Logic diagram:-

Half subtractor:-

 


→ Truth Table

A	B	Borrow	Difference
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

→ Full Subtractor :-

The full subtractor is a combinational of XOR, AND, OR, NOT gates. In a full subtractor the logic circuit should have three inputs and two outputs. The two half subtractors put together gives a full subtractor. The first half subtractor will be C and AB.

Logic diagram :-

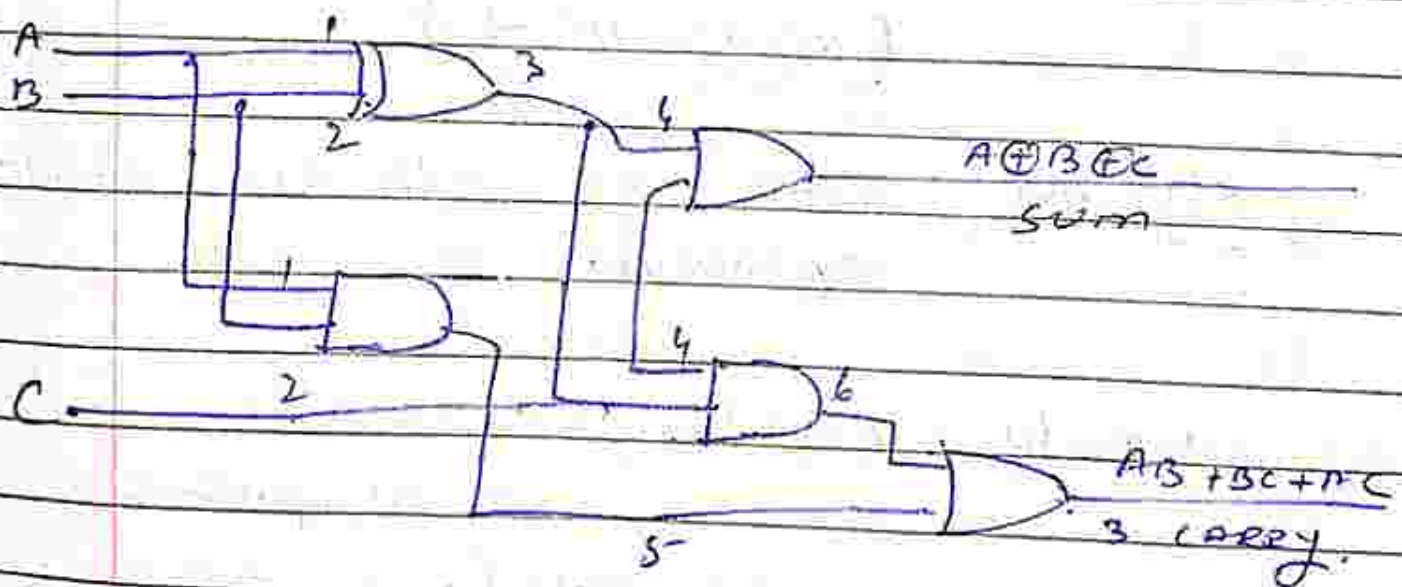

Date: _____
P. No: _____

Truth Table:-

A	B	C	CARRY	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Experiment → 4

⇒ Objective: WAP To add two 16 bit operand.

⇒ Apparatus required:-

micro processor
trainer kit, keyboard.

⇒ program:-

Addition of two 8-bit operands.

Address	Op code	MNEMONIC	Comments
2000H	F8	CLC	clear carry flag
2001H-1	B0 10	MOV AL, 10H	Load AL with 8 bit data.
2003H	B3 20	MOV BL, 20H	Load BL with 8 bit data
2005H	00 D8	ADD AL, BL	Add contents of AL and BL registers.
2007H	CC	INT 3	Interrupt Type 3

```

org 100h
mov al, 10h
mov bl, 10h
add al, bl
mov [2000h], al

```

Experiment-5

Objective :- WAP To add two 16 bit operand.

(A)

program :-

memory	Address	MNEMONICS	Comments
2000	LDA 2050	$A \leftarrow 2050$	
2003	MOV B, A	$B \leftarrow A$	
2004	LDA 2052	$A \leftarrow 2052$	
2007	ADD B	$A \leftarrow A + B$	
2008	STA 3050	$A \rightarrow 3050$	
200B	LDA 2051	$A \leftarrow 2051$	
200E	MOV B, A	$B \leftarrow A$	
200F	LDA 2053	$A \leftarrow 2053$	
2012	ADC B	$A \leftarrow A + B + 1$	
2013	STA 3051	$A \rightarrow 3051$	
2016	HLT	Stop execution	

Explanation :-

LDA 2050 \rightarrow stores the value at 2050 in A (Accumulator)

- 2) `MOV B, A` → stores the value of A into B registers.
- 3) `LDA 2052` → stores the value at 2052 in A.
- 4) `ADD B` → add the contents of B and A and store in A.
- 5) `STA 3050` → stores the value at 2051 in A.
- 6) `MOV B, A` → stores the value of A into registers.
- 7) `LDA 3053` → stores the value at 2053 in A.
- 8) `ADC B` → add the content of B, A and carry from the lower bit addition and store in A.
- 9) `STA 3051` → store the result in memory location 3051.
- 11) `HLT` → stop execution.

Experiment 3-6

→ Objective: - WAP to perform
Arithmetic operation: Subtraction.

→ Apparatus Required: -

micro processor
board kit, Keyboard.

Program:-

Subtraction of two 8-bit operands.

Address	Op code	MNEMONIC	Comments
2000H	F8	CLC	Clear carry flag
2001H	B0 20	MOV AL, 20H	Load AL with 8 bit data
2003H	B3 10	MOV BL, 10H	Load BL with 8 bit data
2005H	29 D8	SUB AL, BL	Subtract content of AL and BL registers.
2007H	CC	INT 3	Interrupt Type 3

→ Subtraction of two 16-bit operands.

Address	Op Code	MNEMONIC	Comments
2000H	F8	CLC	Clear carry flag
2001H	B8 00 20	MOV AX, 200H	Load AX with 16 bit data.
2004H	BB 00 10	MOV BX, 1000H	Load BX with 16 bit data
2007H	29 08	SUB AX, BX	Subtract content of AX & BX registers.
2009H	CC	INT 3	Interrupt Type 3.

Conclusion :-

All the programs are written and o/p are verified.

✓

Experiment - 7

Objective :- NAP to perform multiplication
Arithmetic operation: subtraction.

⇒ Apparatus Required :-

micro processor

trainer kit, keyboard.

multiplication of two 8-bit operands.

<u>address</u>	<u>opcode</u>	<u>mnemonic</u>	<u>comments</u>
2000H	F8	CLC	clear carry flag
2001H	B0 20	MOV BL, 20H	load BL with 8 bit data
2002H	B0 10	MOV AL, 10H	load AL with 8 bit data
2005H	00 D8	ADD AL, BL	multi content of AL and BL registers
2007H	CC	INTC	interrupt type 3

Date: _____

P. No: _____

q/s
mov 100h
mov al, [2000h]
mov bl, [2001h]
mul bl
mov [2000h], ax

Experiment :- 8

Objective :- WAP to perform Arithmetic operation: Division.

Apparatus required :-

micro processor
trainer kit, key board.

org 00h
mov [2000h], 02h;
mov [2001h], 08h;
mov [2002h], 0Fh;
mov al, [2000h];
mov bl, [2002h];
mov cl, [2001h];
mov dl, [2000h];
ret

Roll no. → 0105CS203D03

Date: _____
P. No. _____

Experiment :- 9

Objective :- WAP to perform AND operation over two operands.

Apparatus Required :- micro processor trainer kit, keyboard.

Program :-

```
org 00h  
mov bx, 2000h;  
mov si, 0h  
mov cx, 10h  
li;  
mov ax, [bx*si]  
mov ax  
mov [bx*si], ax;  
inc si  
dec cx;  
Jnz li
```

Date: _____
P. No: _____

Experiment - 10

Objective :- N/A to perform OR operation over two operands.

Experiment:- 11

Date: _____

P. No: _____

Objective:- Map to store 16 Bit data information at 2000h and incrementing value by 01

APPARATUS REQUIRED:- Micro processor trainer kit, keyboard.

program:-

org 100h

MOV AL, [2000H]

MOV CL, 0BH

L1:

ROL AL, 1

JRC L2

DEC CL

JNZ L1

JMP L3:

L2:

MOV [2001H], 00H

RET

L3:

MOV [2001H], 00FFH

RET

Experiment: 12

Objective 3:- WAP to perform more than one operation in one program.

APPARTUS Required:- Micro processor. trainer kit, keyboard.

```
MOV al, 10h  
MOV bl, 5h  
AND al, bl  
MOV [2000h], al
```

```
ADD al, 20h  
MOV [2010h], al
```

==>==

Thank you!!